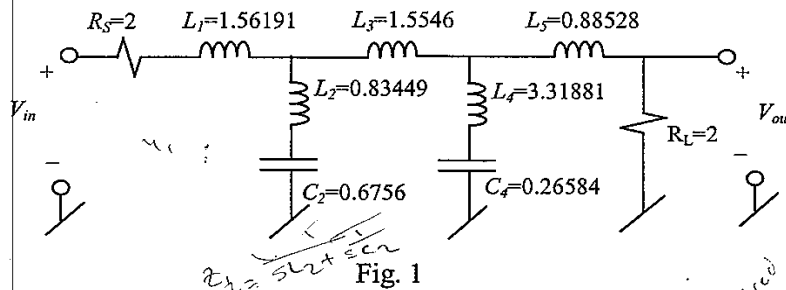


Active Network Synthesis

Midterm

- 1- Using the operational-simulation method, find an opamp-RC circuit corresponding to the elliptic-type lowpass passive prototype in Fig. 1. Considering that cut-off frequency of the passive prototype is $\omega=1\text{rad/s}$, calculate the element values so as the filter cut-off be 20kHz and all the resistances be equal to 1k Ω .



- 2-) A second order bandpass filter with a center frequency of 1MHz and Q of 1 is to be designed using the topology in Fig. 2a. The input signal, I_{in} and the output signal, I_{out} are currents, so the filter will realise a current transfer function. The involved amplifier is a current amplifier with an amplification factor of α , whose defining equations are given as in Fig. 2b:

- a) Determine for what type of t_{AB} ($= I_A / I_B$), the center frequency will be independent of α . Explain why the center frequency is preferred to be independent of α ?

Assume that, the passive network is as in Fig. 2c.

- b) Determine the types of the component.

- c) Find the values of the components.

- d) Determine where to inject the input signal in order to obtain a bandpass response. Draw the overall filter.

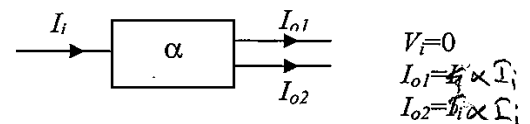
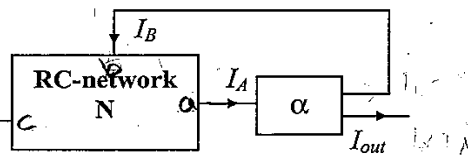


Fig. 2a

Fig. 2b


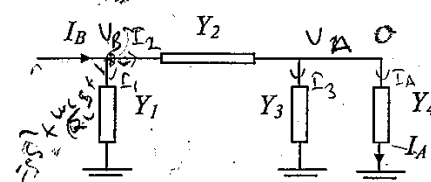


Fig. 2c

$$(V_B - V_A) Y_2 + Y_1 V_B = I_B$$

$$(Y_3 + Y_4) V_A =$$


$$(I_{o1} - I_{o2}) s =$$

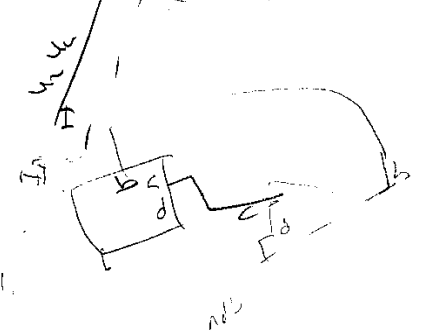

ACTIVE NETWORK SYNTHESIS Final Exam

January 16th, 2006

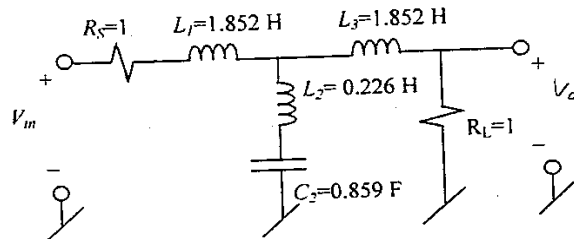- 1) a) Find an OTA-C circuit which simulates the given third-order Chebyshev type lowpass filter whose cut-off angular frequency is 2rad/s.
- b) Determine element values so that the filter cut-off frequency be 10MHz and OTA g_m s be 100 μ S.
- c) Explain how you can convert this circuit into a fully-balanced OTA-C filter.



$$\frac{a_0 a_1}{s^2}$$

$$1 + \frac{q_1}{s} + \frac{q_1 q_0}{s^2}$$

$$s^2 + q_1 s + q_1 q_0$$

2. a) Find the transfer function of the basic circuit in Fig. 2a. Using this circuit, find a second-order Butterworth type lowpass filter ($Q = 1/\sqrt{2}$) based on the signal flow graph in Fig. 2b. (Hint: Find an elementary signal flow graph from the circuit in Fig. 2a. Determine how this type of subgraphs are used to compose the graph in Fig. 2b.)
- b) Determine element values in order to have a cut-off frequency of 1MHz. All caps should be 10pF.

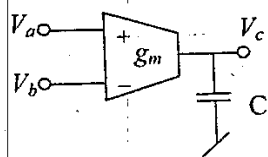
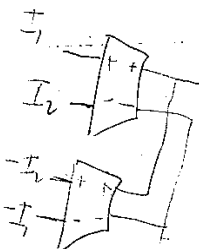


Fig. 2a

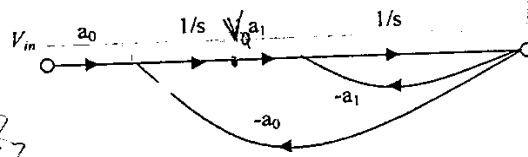


Fig. 2b

3. a) Find z-domain transfer function of the circuit in Fig. 3 and show that the circuit is an integrator.
- b) If the integration constant of the circuit is G_{eq}/C_f find the approximate value of G_{eq} in terms of switching period T and C_G . (Use the following expression: $s = \frac{1}{T} \frac{1-z^{-1}}{z^{-1}}$)
- c) Using this circuit and the graph of Fig. 2b, find a second order Butterworth type lowpass filter whose cut-off frequency is 1MHz. Take switching frequency as 10MHz.

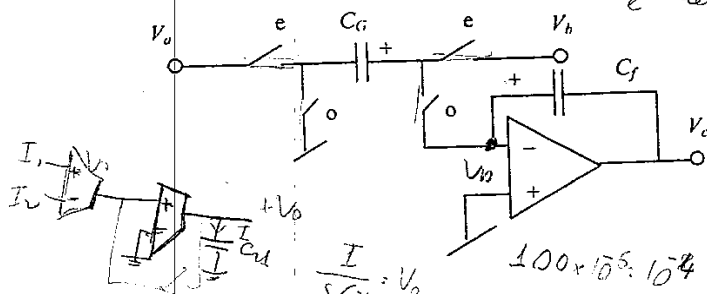


Fig. 3

$$-V_c^e + z^{-\frac{1}{2}} V_c^o = 0$$

$$V_c^e = z^{-\frac{1}{2}} V_c^o$$

$$-V_c^o C_f + z^{-\frac{1}{2}} [(C_f V_c^e) + C_g (V_a^e - V_b^e)] = 0$$

$$V_i g_m = I = V_o \cdot 5 C_{G1}$$

$$\frac{V_o}{V_i} = \frac{5 C_{G1}}{g_m}$$

$$z_{eq} = \frac{1}{s C_G} = 10^4$$

$$10^4 \cdot 5 C_{G1} = 10^4$$

$$5 C_{G1} = 1$$

$$C_{G1} = 0.2 \mu F$$

Filter 2014 copy 2856907

Active Network Synthesis Midterm

December 25th, 2001

- 1- Using the operational-simulation method, find an opamp-RC circuit corresponding to the elliptic-type lowpass passive prototype in Fig. 1. The cut-off frequency is to be 1kHz and the resistances are to be all equal to 1kΩ.

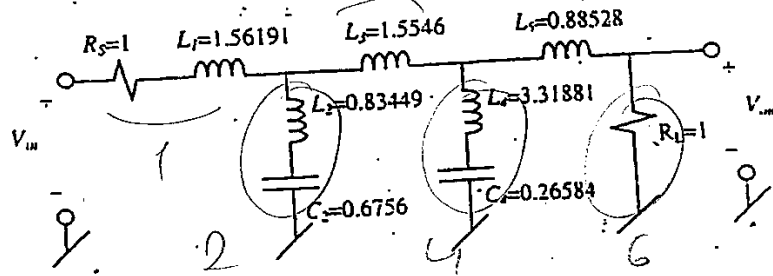


Fig. 1

- 2- a) Find the transfer function of the circuit in Fig. 2. Using this circuit, a second-order Butterworth type filter based on two-integrator loop-topology is to be designed. Find a lowpass filter using 3 OTA and 2 capacitors. Note: The cut-off frequency should be $2\pi \cdot 10^6$ rad/s, all the caps should be 10pF and take all $g_{m,i}$ (except possibly one) equal.

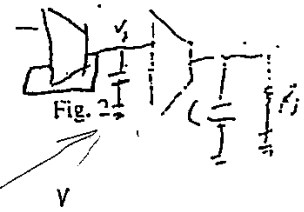
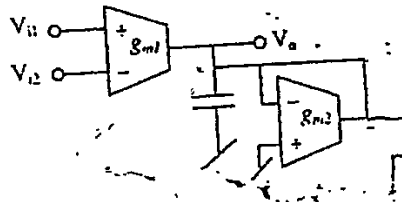


Fig. 2

- b) At high frequencies, OTA transconductance can be modeled as $g_m(s) = \frac{g_m}{1+s/p}$. Find the expression of the nonideal ω_0 and pole-Q in terms of the ideal ones.
Hint: Use the following approximation: $\frac{1}{(1+s/p)^n} \approx 1 - ns/p$
Find a compensation method to reduce the effects of the OTA finite bandwidths. (Hint: In order to insert a zero to the transfer function of the circuit in Fig. 2, use a small valued resistor)

- c) Convert the circuit you have obtained in (a) into a second-order bandpass filter without using any additional component.

$$\begin{aligned}
 V_0 \cdot j\omega &= \frac{V_{01}}{0.1} \\
 V_{01} &= \frac{1}{j\omega} \\
 V_0 \cdot j\omega &= V_{01} \cdot j\omega
 \end{aligned}$$

$$s_k$$

$$1=2$$

$$e^{j\pi \left(\frac{3+2k}{4} \right)}$$

$$k=0,1,2,3$$

$$Q=\frac{1}{\sqrt{2}}$$

$$\omega_0=1$$

$$\frac{1}{s^2 + \sqrt{2}s + 1}$$

$$\Delta = 2 - 4 = -2$$

$$j\sqrt{2}$$

$$\left(s - \frac{j\sqrt{2}}{2} + j\frac{j\sqrt{2}}{2} \right) / s = \frac{-\sqrt{2}j\sqrt{2}}{2}$$

December 17th, 2005

ACTIVE NETWORK SYNTHESIS

Midterm

1-) a) Find the transfer function defined as $H(s) = \frac{V_3}{V_1 - V_2}$ of the circuit in Fig. 1a which employs current conveyor as active element.

b) Using this circuit, realize the signal flow graph of Fig. 1b.

c) Using the circuit obtained in b), a Butterworth type ($Q=1/\sqrt{2}$) second-order lowpass filter with a cut-off frequency of 100KHz is to be designed. Determine passive component values.

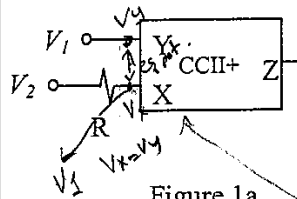


Figure 1a


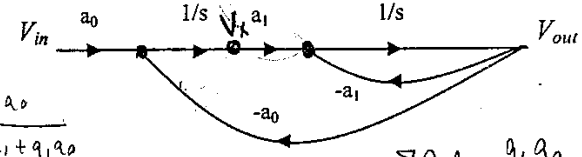


Figure 1b

$$\Sigma P, \Delta := \frac{a_1 a_0}{s^2}$$

$$\Delta = 1 - \left(\frac{-a_1}{s} + \frac{-a_0 a_1}{s^2} \right)$$
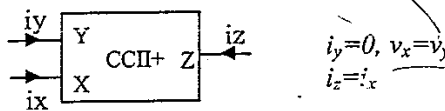
$$1 + \frac{a_1}{s} + \frac{a_1 a_0}{s^2}$$



$$i_y=0, v_x=v_y$$

$$i_z=i_x$$

2-) Find an opamp-RC circuit corresponding to the passive prototype in Fig. 2 using operational simulation method.

b) Assuming that the passive prototype is a lowpass filter with a cut-off frequency of 1rad/sec, design the opamp filter such that the cut-off frequency be 1MHz and all resistors be 1kΩ.

Approx 1Hz den
Filtren
geamige losung

DC blockmp. lowpass


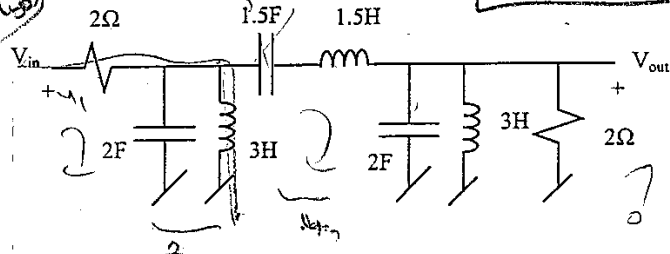
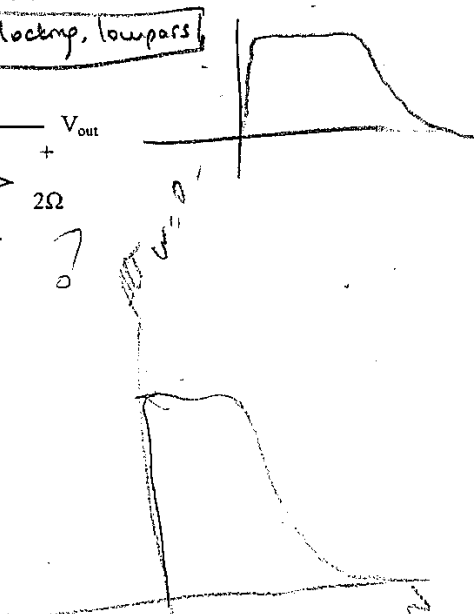


Figure 2

$$a_1, a_0$$

$$2\pi \cdot 10^6$$

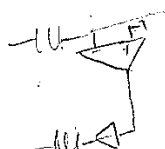

December 26th, 2007

ACTIVE NETWORK SYNTHESIS

Midterm Exam

1) The topology in Fig. 1a consists of an (grounded) RC passive network and a current to voltage converter built around two opamps. Using this topology, a second order Butterworth-type highpass filter with a center frequency of 1MHz and Q of $1/\sqrt{2}$ will be designed.

a) Determine for what type of G_{cb} ($= I_C / V_{out}$), the center frequency will be independent of the opamps finite gains. Show that complex-poles can be realised using this filter (Hint: Express the pole-Q of the system in terms of the parameters of RC-network and R).

Assume that, RC-network is chosen as in Fig. 1b.

b) Determine component types.

✓ b) Determine where to inject the input signal in order to obtain highpass response.

c) Show that the filter realizes highpass characteristic. $\frac{V_s}{V_{out} \text{ bal.}}$

d) Find the values of components assuming that all capacitors are $1\mu F$.

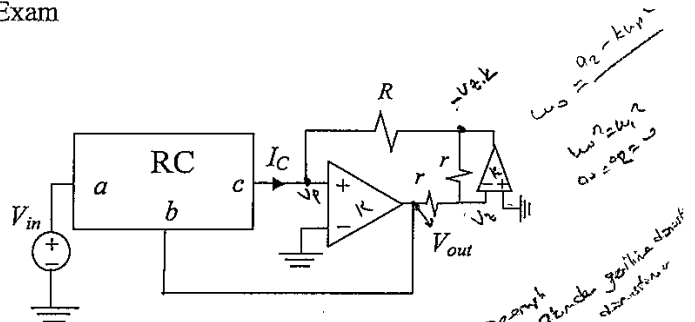


Fig. 1a

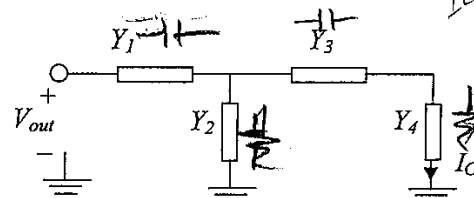


Fig. 1b

2) a) The circuit in Fig. 2 is a second-order lowpass filter with a cut-off frequency of 1 rad/sec. Obtain a fourth-order bandpass filter with a center frequency of 1 rad/sec and $Q=5$ using lowpass-bandpass transformation. Find an OPAMP-RC circuit realising the bandpass filter.

b) Determine the values of passive components in order to have a cut-off frequency of 10MHz. All R 's will be $1k\Omega$.

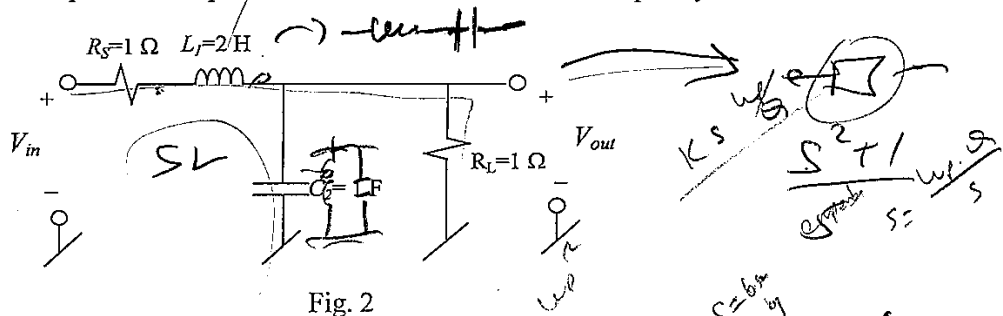


Fig. 2