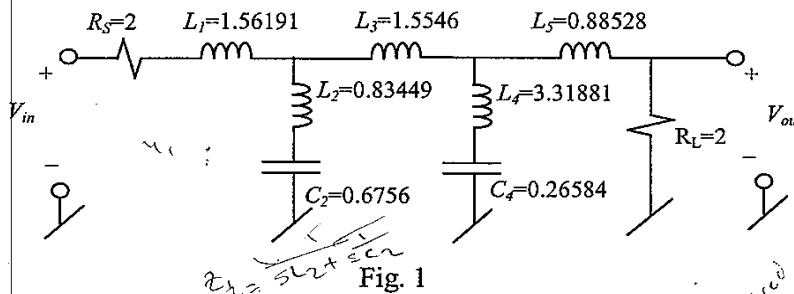


## Active Network Synthesis

### Midterm

- 1- Using the operational-simulation method, find an opamp-RC circuit corresponding to the elliptic-type lowpass passive prototype in Fig. 1. Considering that cut-off frequency of the passive prototype is  $\omega=1\text{rad/s}$ , calculate the element values so as the filter cut-off be 20kHz and all the resistances be equal to  $1\text{k}\Omega$ .



- 2-) A second order bandpass filter with a center frequency of 1MHz and Q of 1 is to be designed using the topology in Fig. 2a. The input signal,  $I_{in}$  and the output signal,  $I_{out}$  are currents, so the filter will realise a current transfer function. The involved amplifier is a current amplifier with an amplification factor of  $\alpha$ , whose defining equations are given as in Fig. 2b.




- a) Determine for what type of  $t_{AB}$  ( $=I_A/I_B$ ), the center frequency will be independent of  $\alpha$ . Explain why the center frequency is preferred to be independent of  $\alpha$ .

Assume that, the passive network is as in Fig. 2c.

- b) Determine the types of the component.

- c) Find the values of the components.

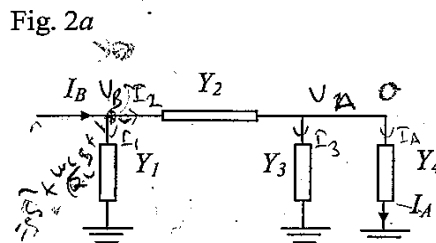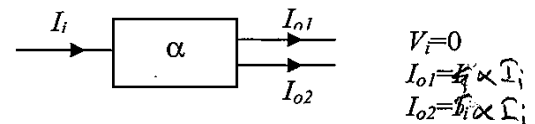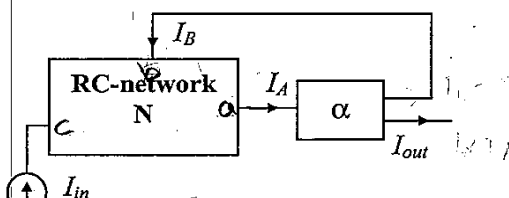
- d) Determine where to inject the input signal in order to obtain a bandpass response. Draw the overall filter.



$$(Y_2 - Y_4) V_B + Y_1 V_A = I_B$$

$$(Y_3 + Y_4) V_A = I_A$$

$$(I_{o1} - I_{o2}) s =$$

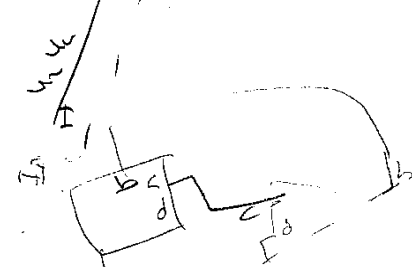

Handwritten notes and equations:

$$I_A = \alpha I_B$$

$$\alpha I_A = \alpha^2 I_B$$

$$I_{out} = \alpha I_A = \alpha^2 I_B$$

$$I_{in} = I_B + I_{out} = I_B + \alpha^2 I_B = I_B(1 + \alpha^2)$$

$$I_{out} = \alpha^2 I_B = \alpha^2 I_{in} / (1 + \alpha^2)$$

$$I_{out} = \alpha^2 / (1 + \alpha^2) I_{in}$$

DEC, 19, 2006

a)  $I_A = t_{AB} I_B + t_{AC} I_{in}$

$I_{out} = \alpha I_A$  ,  $I_B = I_{out}$

$I_{out} = \alpha (t_{AB} I_{out} + t_{AC} I_{in})$


$(1 - \alpha t_{AB}) I_{out} = \alpha t_{AC} I_{in} \Rightarrow \frac{I_{out}}{I_{in}} = \frac{\alpha t_{AC}}{1 - \alpha t_{AB}} = \frac{t_{AC} \alpha}{\frac{1}{\alpha} - t_{AB}}$

$D(s) = \frac{1}{\alpha} - t_{AB} \rightarrow$  EPF filter.

$t_{AB} = \frac{n_{ca}(s)}{d_1(s)} = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + s \frac{\omega_1}{Q_p} + \omega_1^2} \Rightarrow \frac{I_{out}}{I_{in}} = \frac{t_{AC} \alpha}{1 - \alpha \frac{a_2 s^2 + a_1 s + a_0}{s^2 + s \frac{\omega_1}{Q_p} + \omega_1^2}}$

$\omega_0^2 = \frac{a_0 - k_0 \omega_1^2}{a_2 - k_0}$  ,  $k_0 = \alpha$  'den bağımlıdır.  $\omega_0^2 = \omega_1^2$

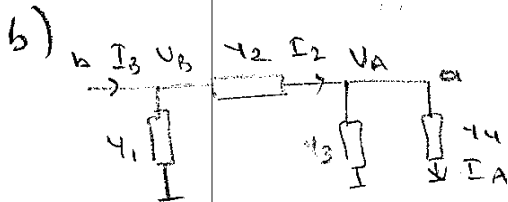$a_0 = a_2 = 0 \Rightarrow$  olarak seçilmeli.  $\Rightarrow \frac{a_1 s}{s^2 + s \frac{\omega_1}{Q_p} + \omega_1^2}$



$(Y_3 + Y_4) V_A = I_2$  ,  $I_A = Y_4 V_A$

$(Y_3 + Y_4) \frac{I_A}{Y_4} = I_2$

$I_B = V_B Y_1 + \frac{(Y_3 + Y_4) I_A}{Y_4}$

$I_B = \frac{(Y_3 + Y_4 + Y_2) Y_1 + Y_2 (Y_3 + Y_4)}{Y_2 Y_4} I_A$

$\frac{I_A}{I_B} = \frac{Y_2 Y_4}{(Y_3 + Y_4 + Y_2) Y_1 + Y_2 (Y_3 + Y_4)}$

$Y_2 = sC_2$  ,  $Y_4 = G_4$  ,  $Y_3 = sC_3$  ,  $Y_1 = G_1$

$t_{AB} = \frac{I_A}{I_B} = \frac{a_1 s}{s^2 + s \frac{\omega_1}{Q_p} + \omega_1^2}$

$t_{AB} = \frac{I_A}{I_B} = \frac{sC_2 G_4}{(sC_3 + G_4 + sC_2) G_1 + sC_2 (sC_3 + G_4)}$

DEC 19, 2006

②

$$t_{AB} = \frac{I_A}{I_B} = \frac{s C_2 G_4}{s^2 C_2 C_3 + s(C_3 G_1 + C_2 G_1 + C_2 G_4) + G_1 G_4}$$

$$t_{AB} = \frac{s G_4 / C_3}{s^2 + \frac{(C_3 + C_2) G_1 + C_2 G_4}{C_2 C_3} + \frac{G_1 G_4}{C_2 C_3}}$$

$$\omega_0^2 = \frac{G_1 G_4}{C_2 C_3} = (10^6 \cdot 2\pi)^2$$

$$\frac{\omega_p}{Q_p} = \frac{(C_3 + C_2) G_1 + C_2 G_4}{C_2 C_3} \Rightarrow Q_p = 1 \Rightarrow \sqrt{\frac{G_1 G_4}{C_2 C_3}} = \frac{(C_3 + C_2) G_1 + C_2 G_4}{C_2 C_3}$$

$$C_2 = C_3 = 10 \text{ pF}$$

$$= 10^3 \cdot 10^{-24} \cdot 10^{12} \cdot 4\pi^2 = 4\pi^2 \cdot 10^{-10}$$

$$\frac{2G_1 + G_4}{C} = 2\pi \cdot 10^6 \Rightarrow 2G_1 + G_4 = 2\pi \cdot 10^{-5}$$

$$\frac{2 \cdot (10^2 \cdot 10^{-10})}{G_4} + G_4 = 2\pi \cdot 10^{-5} \Rightarrow G_4^2 - 2\pi \cdot 10^{-5} G_4 + 8\pi^2 \cdot 10^{-10} = 0$$

$$G_4 =$$

$$\frac{I_{out}}{I_{in}} = \frac{\alpha t_{AC}}{1 - \alpha t_{AB}} = \frac{\alpha t_{AC}}{1 - \alpha \left( \frac{a_2 s^2 + a_1 s + a_0}{s^2 + \frac{\omega_1}{Q_p} s + \omega_1^2} \right)} = \frac{\alpha t_{AC} \cdot (s^2 + \frac{\omega_1}{Q_p} s + \omega_1^2)}{(s^2 + \frac{\omega_1}{Q_p} s + \omega_1^2) - \alpha (a_2 s^2 + a_1 s + a_0)}$$

$$t_{AB} = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + \frac{\omega_1}{Q_p} s + \omega_1^2}$$



$$= \frac{\alpha t_{AC} (s^2 + \frac{\omega_1}{Q_p} s + \omega_1^2)}{(1 - \alpha a_2) s^2 + \left( \frac{\omega_1}{Q_p} - \alpha a_1 \right) s + \omega_1^2 - \alpha a_0}$$

$$\omega^2 = \frac{\omega_1^2 \alpha a_0}{1 - \alpha a_2}$$

$$a_0 = a_2 = 0$$

$$a_0 = \omega_1^2 a_1$$

Dec 19 2006 Mid km  
Surv 2

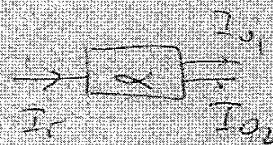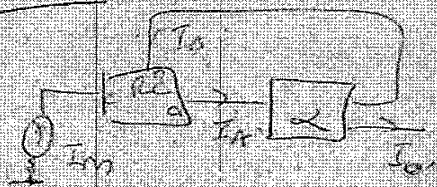

$$V_1 = 0$$

$$I_{o1} = I_{o2} = I_o \alpha$$

(a)

$$I_A = t_{ab} \cdot I_B + t_{ac} \cdot I_m$$

$$\frac{I_o}{\alpha} = I_B = I_A \alpha$$

$$\frac{I_o}{\alpha} = t_{ab} \cdot I_o + t_{ac} \cdot I_m$$

$$I_o \left( \frac{1}{\alpha} - t_{ab} \right) = t_{ac} I_m$$

$$H(s) = \frac{I_o}{I_m} = \frac{t_{ac} \alpha}{1 - \alpha t_{ab}}$$

$$t_{ab} = \frac{n_{ab}}{d(s)} = \frac{a_0 s^2 + a_1 s + a_2}{s^2 + \frac{\omega_1}{Q} s + \omega_0^2}$$

$$H(s) = \frac{\frac{\omega_0}{Q} s}{s^2 + \frac{\omega_1}{Q} s + \omega_0^2}$$

$$\rightarrow = 1 - \alpha t_{ab} = 1 - \alpha \frac{n_{ab}}{d(s)}$$

$$= d(s) - \alpha n_{ab}$$

$$s^2 + \frac{\omega_1}{Q} s + \omega_0^2 = s^2 + \frac{\omega_1}{Q} s + \omega_0^2 - \alpha (a_0 s^2 + a_1 s + a_2)$$

$$s^2 + \frac{\omega_1}{Q} s + \omega_0^2 = \frac{s^2 + (\frac{\omega_1}{Q} - a_1 \alpha) s + (\omega_0^2 - \alpha a_2)}{(1 - \alpha a_0 \alpha)}$$

$$a_0 = a_2 = 0 \text{ then } \omega_1^2 = \omega_0^2 \Rightarrow \omega_1 = \omega_0$$

$$\frac{\omega_1}{Q} - a_1 \alpha = \frac{\omega_0}{Q} \Rightarrow \frac{\omega_0}{Q} = \frac{\omega_0}{Q} - \frac{\omega_0 \alpha}{Q} \Rightarrow \frac{\omega_0 \alpha}{Q} = \frac{a_1 \alpha}{Q}$$

$$t_{ab} = \frac{\frac{\omega_0}{Q} s}{s^2 + \frac{\omega_1}{Q} s + \omega_0^2}$$

$$\frac{a_1 \alpha}{Q} = \frac{a_1 \alpha}{Q}$$

(1)



b)

$$I_B = I_1 + I_3 + I_A \quad \frac{I_3}{Y_3} = \frac{I_A}{Y_4}$$

$$I_B(I) + I_A\left(\frac{Y_3}{Y_4} - 1\right)$$

$$\frac{I_1}{Y_1} = \frac{I_2}{Y_2} + \frac{I_A}{Y_4}$$

$$\frac{I_1}{Y_1} = (I_3 + I_A) \frac{1}{Y_2} + \frac{I_A}{Y_4}$$

$$\frac{I_1}{Y_1} = I_A\left(\frac{Y_3}{Y_4} - 1\right) \frac{1}{Y_2} + \frac{I_A}{Y_4}$$

$$I_A = I_A \left[ \frac{Y_1}{Y_4} + \left(\frac{Y_3}{Y_4} - 1\right) \frac{Y_1}{Y_2} \right]$$

$$I_B = I_A \left\{ \left(\frac{Y_3}{Y_4} - 1\right) + \frac{Y_1}{Y_4} + \left(\frac{Y_3 + Y_1}{Y_4}\right) \frac{Y_1}{Y_2} \right\}$$

$$\frac{I_A}{I_B} = \frac{\frac{Y_3 + Y_1}{Y_4} + \frac{Y_1}{Y_4} + \frac{Y_3 + Y_1}{Y_4} \frac{Y_1}{Y_2}}{1}$$

$$\frac{I_A}{I_B} = \frac{Y_1 Y_2}{Y_1 Y_2 + Y_1 Y_3 + Y_2 Y_4 + Y_2 Y_3 + Y_1 Y_4}$$

$$\rightarrow Y_3(Y_1 + Y_2) + Y_4(Y_1 + Y_2) + Y_1 Y_2$$

$$(Y_1 + Y_2)(Y_3 + Y_4) + Y_1 Y_2$$

$$\frac{I_A}{I_B} = \frac{Y_1 Y_2}{(Y_1 + Y_2)(Y_3 + Y_4) + Y_1 Y_2}$$

$$Y_1 = G_1 \quad Y_2 = sC_2 \quad Y_3 = sC_3 \quad Y_4 = G_4$$

$$= \frac{sC_2 G_4}{(G_1 + sC_2)(sC_3 + G_4) + G_1 sC_2} = \frac{sC_2 G_4}{s^2 C_2 C_3 + s(C_2 G_4 + G_1 C_3 + G_1 C_2) + G_1 G_4}$$

$$\frac{s \cdot G_4 / C_3}{s^2 + (C_2 G_4 + G_1 C_3 + G_1 C_2)} \cdot \frac{G_1 G_4}{C_2 C_3}$$



$$\omega_0 = \sqrt{\frac{G_1 G_4}{C_2 C_3}}$$

$$\frac{\omega_0}{q_p} = \frac{G_4}{C_3} \Rightarrow q_2 = \sqrt{\frac{G_1 G_4 \cdot C_4}{C_2 C_3 G_4}} = \sqrt{\frac{G_1 C_3}{C_2 G_4}}$$

$$\frac{\omega_0}{q_p} = \omega \Rightarrow q_p = \sqrt{\frac{G_1 G_4}{C_2 C_3} \cdot \frac{\sqrt{C_2 C_3}}{C_2 G_4 + G_1 C_3 + G_1 C_2}}$$

$$\frac{\omega_0}{q_p} = \omega$$

$$Q = \dots$$

$$\omega_0 = 6.28 \times 10^4$$

$$Q = 1$$

$$C_1 = C_2 = C_3 = C_4 = 1 \mu F \text{ olsun}$$

$$3.94 \times 10^{13} = \frac{G_1 G_4}{10^{-24}} \Rightarrow G_1 G_4 = 3.94 \times 10^{-11}$$

$$G_1 = 3.94 \times 10^{-11} \Rightarrow R_1 = 2.53 k\Omega$$

$$G_4 = 1 \times 10^{-7} \Rightarrow R_2 = 10 M\Omega$$

$$q_2 = \sqrt{3.94 \times 10^{13}}$$

$$q_2 = 62.76$$

$$q_p = \frac{\sqrt{G_1 G_4 \cdot 10^{-24}}}{10^{-12} (10^{-7} + 2 \times 3.94 \times 10^{-11})}$$

$$q_p = \frac{6.27 \times 10^{-18}}{7.88 \times 10^{-16}} = 7.95 \times 10^{-3}$$

$$Q = 1 \Rightarrow q_2 - q_p \omega = q_p q_2$$


$$-q_p \omega = q_2 (q_p - 1)$$

$$\omega = \frac{q_2 (1 - q_p)}{q_p} \Rightarrow \frac{(62.76)(1 - 7.95 \times 10^{-3})}{7.95 \times 10^{-3}}$$

$$\omega = 7.86 k\Omega$$




(d)

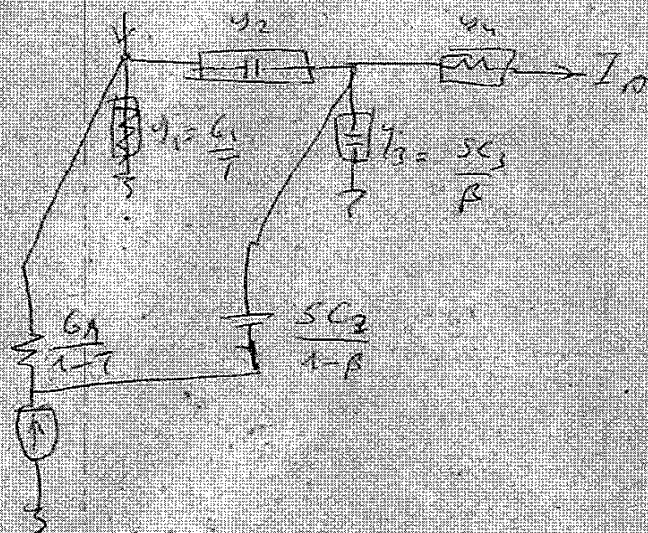

# ACTIVE NETWORK SYNTHESIS Final Exam

January 16th, 2006

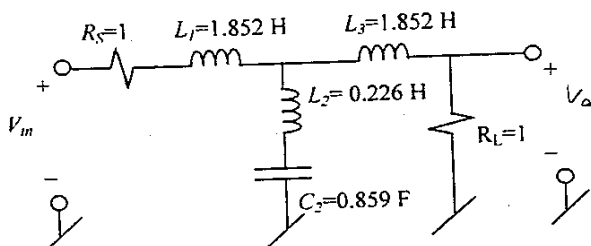- 1) a) Find an OTA-C circuit which simulates the given third-order Chebyshev type lowpass filter whose cut-off angular frequency is 2rad/s.
- b) Determine element values so that the filter cut-off frequency be 10MHz and OTA  $g_m$ s be 100 $\mu$ S.
- c) Explain how you can convert this circuit into a fully-balanced OTA-C filter.



$$\frac{a_0 a_1}{s^2}$$

$$1 + \frac{a_1}{s} + \frac{a_2}{s^2}$$

$$s^2 + 3.5s + 9.90$$

2. a) Find the transfer function of the basic circuit in Fig. 2a. Using this circuit, find a second-order Butterworth type lowpass filter ( $Q=1/\sqrt{2}$ ) based on the signal flow graph in Fig. 2b. (Hint: Find an elementary signal flow graph from the circuit in Fig. 2a. Determine how this type of subgraphs are used to compose the graph in Fig. 2b.)

- b) Determine element values in order to have a cut-off frequency of 1MHz. All caps should be 10pF.

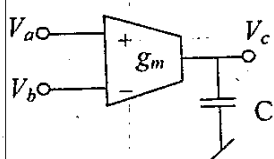
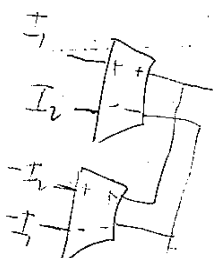


Fig. 2a

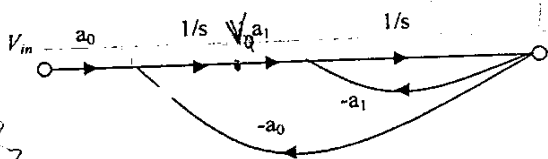


Fig. 2b

3. a) Find z-domain transfer function of the circuit in Fig. 3 and show that the circuit is an integrator.
- b) If the integration constant of the circuit is  $G_{eq}/C_f$  find the approximate value of  $G_{eq}$  in terms of switching period  $T$  and  $C_G$ . (Use the following expression:  $s = \frac{1}{T} \frac{1-z^{-1}}{z^{-1}}$ )
- c) Using this circuit and the graph of Fig. 2b, find a second order Butterworth type lowpass filter whose cut-off frequency is 1MHz. Take switching frequency as 10MHz.

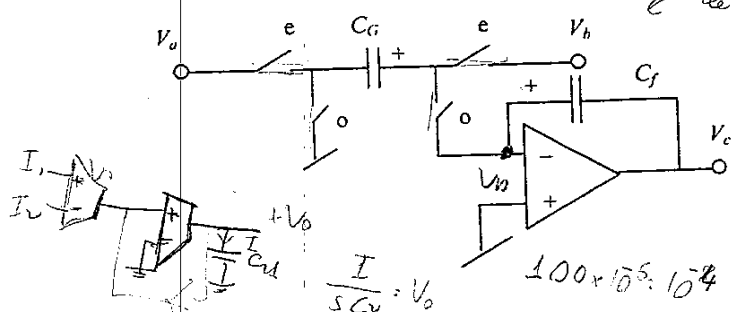


Fig. 3

even  $C_f$

$$-V_c^e + z^{-\frac{1}{2}} V_c^o = 0$$

$$V_c^e = z^{-\frac{1}{2}} V_c^o$$

odd  $C_f$

$$-V_c^o + z^{-\frac{1}{2}} V_c^e = 0$$

$$C_G (V_a^e - V_b^e) = 0$$

Handwritten notes:

$$V_i \cdot g_m = I = V_o \cdot s C_G$$

$$\frac{I}{s C_G} = V_o$$

$$z_{eq} = \frac{1}{s C_G} = \frac{1}{10^6 \cdot 10^{-14}} = 10^8$$






**İTÜ**  
**ELEKTRİK - ELEKTRONİK FAKÜLTESİ**

Soru	1	2	3	4	5	6	7	8	Toplam
Not									


Tarih : ..... / ..... / .....  
Bölüm : .....  
Ders : .....  
No : .....  
Adı Soyadı : .....  
İmzası : .....

Jan 16 2006


1)

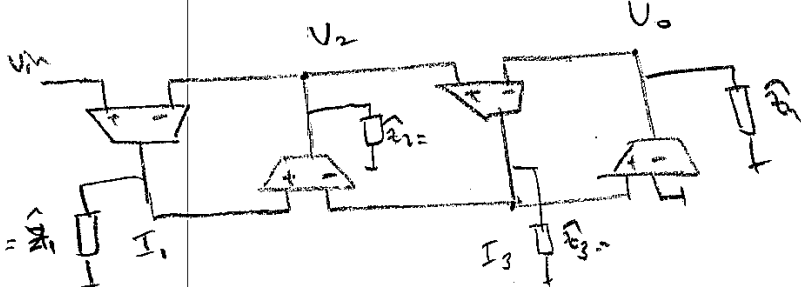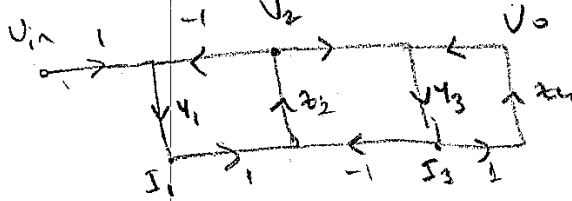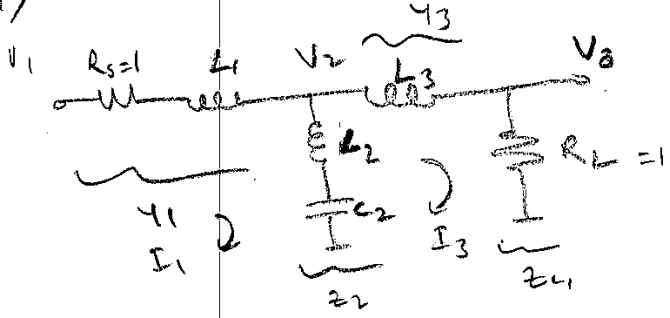

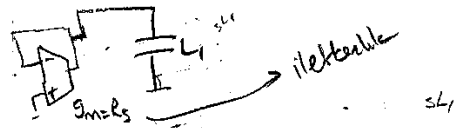
$$\hat{Z}_1 = Z_1 = R_s + sL_1 = \frac{1}{s} + \frac{1}{sL_1}$$



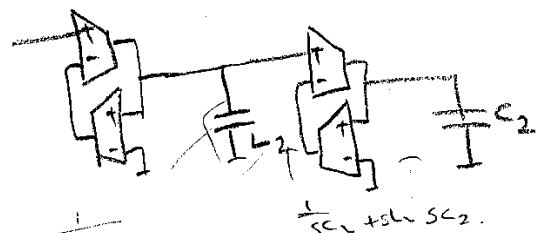
$$\hat{Z}_2 = Z_2 = sL_2 + \frac{1}{sC_2}$$



$$\hat{Z}_3 = Z_3 = \frac{1}{sL_3}$$

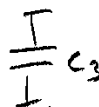


$$\hat{Z}_4 = R_4$$

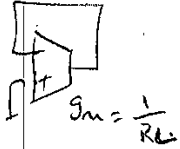

→

$$(V_a - V_b) g_m = V_c$$
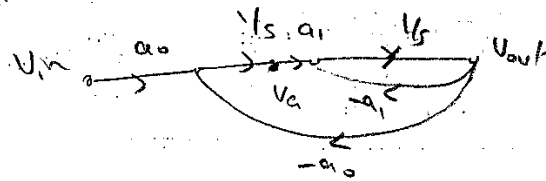
$$\frac{V_c}{V_a - V_b} = \frac{g_m}{sC}$$



$$\frac{V_a a_1 - V_{out} a_1}{s} = V_{out}$$


$$\frac{V_a a_1 - a_1 V_{out}}{s} = V_{out}$$

$$\frac{(V_a - V_{out}) a_1}{s} = V_{out}$$

$$\frac{a_1}{s} (V_a - V_{out}) = V_{out}$$

$$V_a = s V_{out}$$
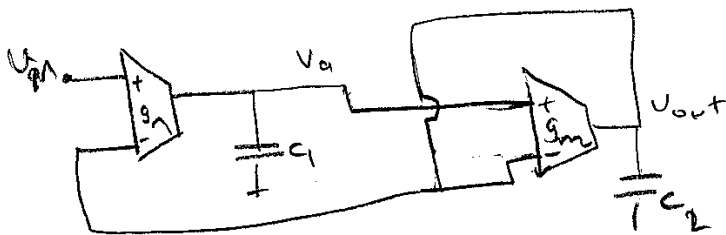
$$V_a = \frac{V_{in} a_0 - V_{out} a_0}{s}$$



$$a_0 = \frac{g_{m1}}{C_1}$$

$$a_1 = \frac{g_{m2}}{C_2}$$


$$V_{in} \frac{a_0}{s^2 + \dots + 1}$$

$$\frac{(V_{in} a_0 - V_{out} a_0) a_1}{s} = V_{out}$$

$$\frac{\sqrt{g_{m1} g_{m2}}}{C} = 2\pi \cdot 10^6$$

$$\frac{V_{in} a_0 a_1 - V_{out} (a_0 a_1) - s a_1 V_{out}}{s} = V_{out}$$
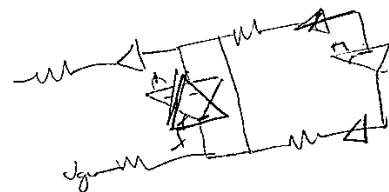
$$\frac{V_{in} a_0 a_1}{s^2 + s a_1 + a_0 a_1} = \frac{V_{out}}{V_{in}}$$



$$a_1 = \sqrt{2}$$


$$a_0 a_1 = 2\pi \cdot 10^6$$

**İ.T.Ü.**  
**ELEKTRİK ELEKTRONİK FAKÜLTESİ**

Soru	1	2	3	4	5	6	7	8	Topl
Not									

Tarih : .....  
Bölüm : .....  
Ders : .....  
No : .....  
Adı, Soyadı : .....  
İmzası : .....

2005

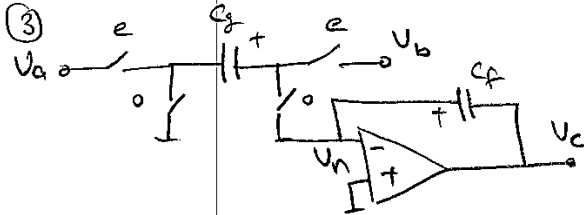

*Jan 16 2006*

node - n  
even - times

$$(V_n^e - V_c^e) C_f - z^{-1/2} (V_n^e - V_c^e) = 0 \Rightarrow \underline{V_c^e = z^{-1/2} V_c^e} \Rightarrow \text{full-clock signal}$$

odd - times

$$(V_n^e - 0) C_g + (V_n^e - V_c^e) C_f - z^{-1/2} C_g (V_b^e - V_a^e) - z^{-1/2} C_f (V_n^e - V_c^e) = 0$$

$$\left( \frac{-1}{z^{-1/2}} + z^{-1/2} \right) C_f V_c^e = z^{-1/2} C_g (V_b^e - V_a^e)$$

$$\left( \frac{z^{-1} - 1}{z^{-1/2}} \right) C_f V_c^e = z^{-1/2} C_g (V_b^e - V_a^e)$$

$$\frac{V_c^e}{(V_b^e - V_a^e)} = - \left( \frac{z^{-1}}{1 - z^{-1}} \right) \cdot \frac{C_g}{C_f}$$


$$b) \frac{V_c^e}{V_b^e - V_a^e} = - \frac{C_g}{5T C_f} \Rightarrow \frac{-C_g}{T C_f} = \frac{G_{eq}}{C_f} \Rightarrow \underline{\underline{G_{eq} = \frac{C_g}{T}}}$$



$$c) \frac{a_0 (V_{in} - V_{out})}{s} = V_a$$

$$\frac{a_1 (V_a - V_{out})}{s} = V_{out}$$
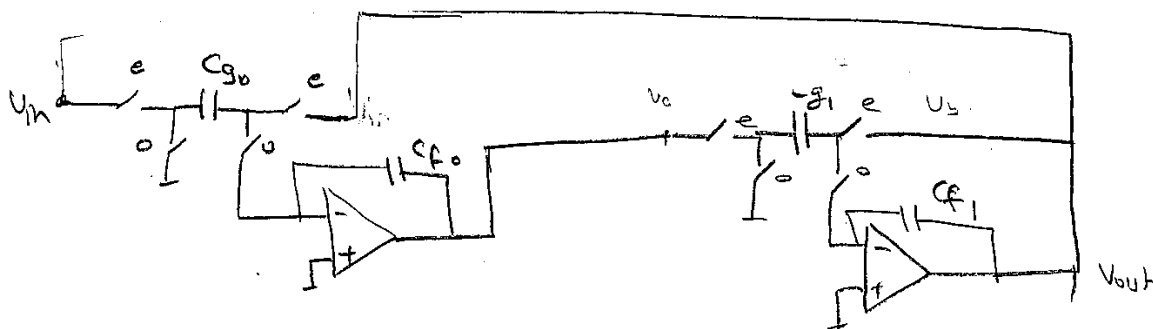
$$\frac{V_{out}}{V_{in}} = \frac{a_0 a_1}{s^2 + a_1 s + a_1 a_0}$$



$$a_0 = \frac{G_{eq0}}{C_f} = \frac{C_{g1}}{T \cdot C_f}$$

$$a_1 = \frac{G_{eq1}}{C_f}$$

$$a_1 a_0 = 2\pi \cdot 10^6$$

$$\frac{\omega_p}{\omega_f} = \frac{\sqrt{a_1 a_0}}{a_1} = \frac{1}{\sqrt{2}} \Rightarrow \frac{a_0}{a_1} = \frac{1}{2} \Rightarrow a_1 = 2a_0$$

$$G_{eq1} = 2G_{eq0}$$

$$C_{g1} = 2C_{g0}$$

$$\frac{\sqrt{a_1 a_0}}{\omega_p} = \frac{1}{\sqrt{2}} \Rightarrow \frac{\omega_p}{\omega_f} = \frac{1}{\sqrt{2}}$$

$$\frac{2C_{g0}^2}{T^2 C_f^2} = 2\pi \cdot 10^6 \Rightarrow \frac{\sqrt{2} C_{g0}}{T C_f} = 2\pi \cdot 10^6$$

$$C_f = 10 \text{ pF}$$

$$C_{g0} = \frac{2\pi \cdot 10^{-6} \cdot 10^{-7}}{\sqrt{2} \cdot 10 \cdot 10^{-12}} = 4.44 \text{ pF}$$

$$C_{g1} = 8.88 \text{ pF}$$

Filter paper copy 2856907

# Active Network Synthesis Midterm

December 25th, 2001

- 1- Using the operational-simulation method, find an opamp-RC circuit corresponding to the elliptic-type lowpass passive prototype in Fig. 1. The cut-off frequency is to be 1kHz and the resistances are to be all equal to 1kΩ.

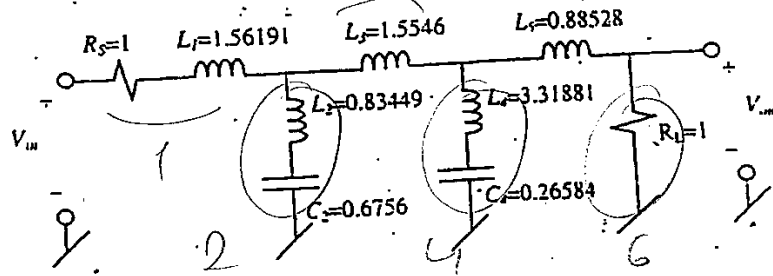


Fig. 1

- 2- a) Find the transfer function of the circuit in Fig. 2. Using this circuit, a second-order Butterworth type filter based on two-integrator loop-topology is to be designed. Find a lowpass filter using 3 OTA and 2 capacitors.  
Note: The cut-off frequency should be  $2\pi \cdot 10^6$  rad/s, all the caps should be 10pF and take all  $g_{m,i}$  (except possibly one) equal.

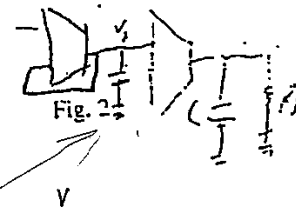
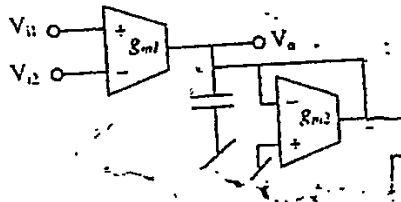


Fig. 2

- b) At high frequencies, OTA transconductance can be modeled as  $g_m(s) = \frac{g_m}{1+s/p}$ . Find the expression of the nonideal  $\omega_0$  and pole-Q in terms of the ideal ones.  
Hint: Use the following approximation:  $\frac{1}{(1+s/p)^n} \approx 1 - ns/p$   
Find a compensation method to reduce the effects of the OTA finite bandwidths. (Hint: In order to insert a zero to the transfer function of the circuit in Fig. 2, use a small valued resistor)

- c) Convert the circuit you have obtained in (a) into a second-order bandpass filter without using any additional component.

$$R_1 = \frac{1}{L_1}$$

$$V_0 \cdot j\omega = \frac{1}{0.1}$$

$$V_{01} = \frac{1}{j\omega \cdot 1}$$

$$V_0 \cdot j\omega = V_{01} \cdot j\omega$$



$$\frac{j\omega (1 - \frac{1}{p})}{j\omega (1 - \frac{1}{p}) - 1}$$

**İTÜ**  
**ELEKTRİK - ELEKTRONİK FAKÜLTESİ**

Soru	1	2	3	4	5	6	7	8	Toplam
Not									

Tarih : ..... / ..... / .....  
Bölüm : .....  
Ders : .....  
No : .....  
Adı Soyadı : .....  
İmzası : .....


⊕ 2001 Midterm Gözönleri ⊕

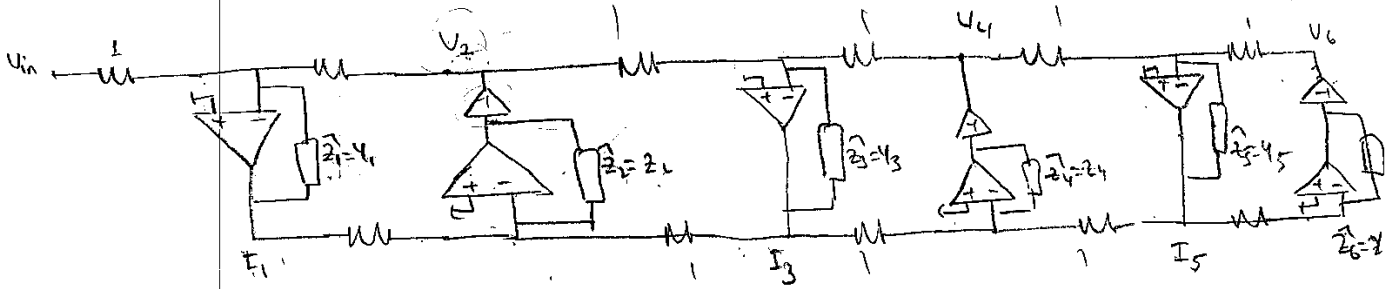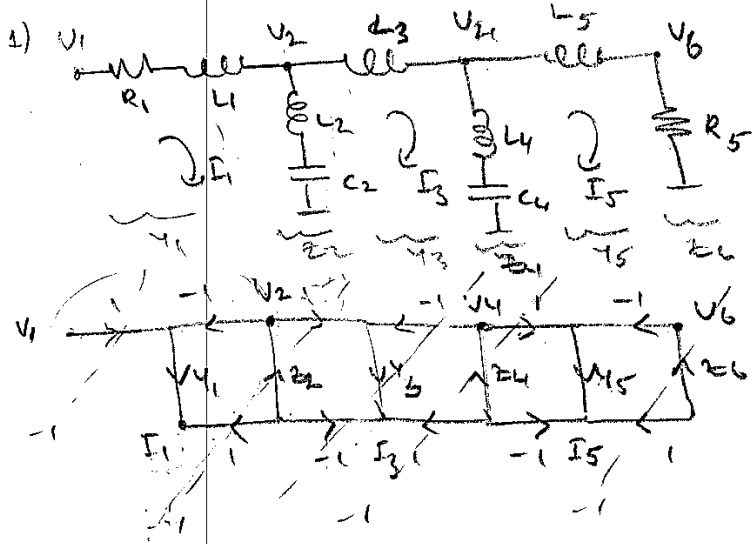


$$\hat{Z}_1 = Y_1 = \frac{1}{R_1 + sL_1}$$



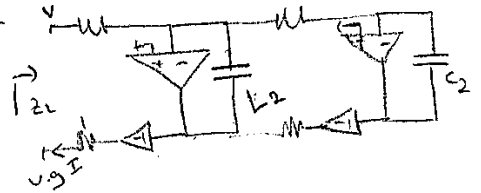
$$\hat{Z}_2 = Z_2 = \frac{1}{sC_2} + sL_2$$



$$\hat{Z}_3 = Y_3 = \frac{1}{sL_3}$$

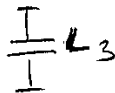
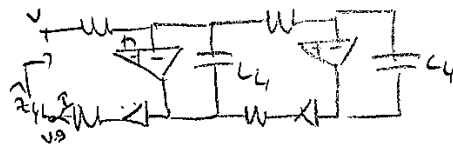
$$\hat{Z}_4 = Z_4 = \frac{1}{sC_4} + sL_4$$



$$\hat{Z}_5 = Y_5 = \frac{1}{sL_5} \Rightarrow \frac{1}{s} L_5$$

$$\hat{Z}_6 = Z_6 = R_5$$





2)

$$(V_{i1} - V_{i2}) g_{m1} = V_o (g_{m2} + sC) \Rightarrow \frac{V_o}{V_{i1} - V_{i2}} = \frac{-g_{m1}}{g_{m2} + sC}$$

$$V_o g_{m3} = sC_2 V_{out} \Rightarrow \frac{sC_2}{g_{m3}} V_{out} = \frac{(V_{in} - V_{out}) g_{m1}}{(g_{m2} + sC)}$$

$$V_{out} \left( \frac{sC_2}{g_{m3}} + \frac{g_{m1}}{(g_{m2} + sC)} \right) = \frac{V_{in} g_{m1}}{g_{m2} + sC} \Rightarrow \frac{V_{out}}{V_{in}} = \frac{g_{m1}}{g_{m2} + sC} \cdot \frac{(g_{m2} + sC) g_{m3}}{(g_{m2} + sC)(sC_2) + g_{m1} g_{m3}}$$

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} g_{m3}}{s^2 C_1 C_2 + s(g_{m2} C_2) + g_{m1} g_{m3}} = \frac{g_{m1} g_{m3} / C_1 C_2}{s^2 + s \frac{g_{m2}}{C_1} + \frac{g_{m1} g_{m3}}{C_1 C_2}}$$

$$\sqrt{\frac{g_{m1} g_{m3}}{C_1 C_2}} = 2\pi \cdot 10^6 \quad C_1 = C_2 = 10 \text{ pF} \Rightarrow g_{m1} = g_{m3} \Rightarrow \frac{g_m}{C} = 2 \cdot \pi \cdot 10^6 \Rightarrow g_m = 2\pi \cdot 10^{-6} = 62.83 \mu\text{S}$$

$$\frac{\omega_p}{Q_p} = \frac{g_{m2}}{C_1} \Rightarrow Q_p = \sqrt{\frac{g_{m1} g_{m3} C_1}{C_1 C_2 g_{m2}}} \Rightarrow \sqrt{\frac{g_{m1} g_{m3} C_1}{C_2}} \cdot \frac{1}{g_{m2}} = \frac{1}{Q_p} \Rightarrow \frac{g_m}{g_{m2}} = \frac{1}{\sqrt{2}} \Rightarrow g_{m2} = 88.86 \mu\text{S}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{g_{m1}^2}{C^2} (1 + s^2/P_2 - 2s/P_1)}{s^2 + s \frac{g_{m2}}{C} (1 - \frac{s}{P_2}) + \frac{g_{m1}^2}{C^2} (1 + s^2/P_2 - 2s/P_1)}$$

$$= \frac{\frac{g_{m1}^2}{C^2 P_1^2} s^2 + \frac{2g_{m1}^2}{C^2 P_1} s + \frac{g_{m1}^2}{C^2}}{s^2 \left( 1 + \frac{g_{m1}^2}{C^2 P_1^2} - \frac{g_{m2}}{C P_2} \right) + s \left( \frac{g_{m1}^2}{C} - \frac{2g_{m1}^2}{C^2 P_1} \right) + \frac{g_{m1}^2}{C^2}}$$

$$= \frac{g_{m1}^2}{C^2} \cdot \frac{s^2 + \frac{2}{P_1} s + 1}{s^2 \left( 1 + \frac{g_{m1}^2}{C^2 P_1^2} - \frac{g_{m2}}{C P_2} \right) + s \left( \frac{g_{m1}^2}{C} - \frac{2g_{m1}^2}{C^2 P_1} \right) + \frac{g_{m1}^2}{C^2}}$$

$$s_k$$

$$1=2$$

$$e^{j\pi \left( \frac{3+2k}{4} \right)}$$

$$k=0,1,2,3$$

$$Q=\frac{1}{\sqrt{2}}$$

$$\omega_0=1$$

$$\frac{1}{s^2 + \sqrt{2}s + 1}$$

$$\Delta = 2 - 4 = -2$$

$$j\sqrt{2}$$

$$\left( s - \frac{j\sqrt{2}}{2} + j\frac{j\sqrt{2}}{2} \right) / s = \frac{-\sqrt{2}j\sqrt{2}}{2}$$

December 17th, 2005

## ACTIVE NETWORK SYNTHESIS

### Midterm

1-) a) Find the transfer function defined as  $H(s) = \frac{V_3}{V_1 - V_2}$  of the circuit in Fig. 1a which employs current conveyor as active element.

✓

b) Using this circuit, realize the signal flow graph of Fig. 1b.

c) Using the circuit obtained in b), a Butterworth type ( $Q=1/\sqrt{2}$ ) second-order lowpass filter with a cut-off frequency of 100KHz is to be designed. Determine passive component values.

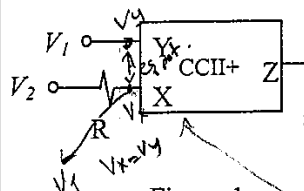


Figure 1a

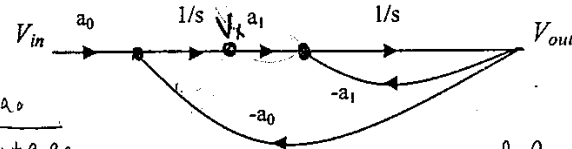


Figure 1b

$$S_n = \frac{S}{2\pi \cdot 10^6}$$

$$R_n = \frac{R}{10^4}$$

$$V_3 = \frac{1}{sRC} (V_1 - V_2)$$

$$\frac{1}{sRC}$$

$$\frac{1}{sRC}$$

$$\frac{1}{sRC} \cdot \frac{R}{10^4} \cdot \frac{1}{2\pi \cdot 10^6} \cdot \frac{1}{sRC}$$

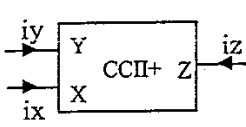


Figure 2

2-) Find an opamp-RC circuit corresponding to the passive prototype in Fig. 2 using operational simulation method.

b) Assuming that the passive prototype is a lowpass filter with a cut-off frequency of 1rad/sec, design the opamp filter such that the cut-off frequency be 1MHz and all resistors be 1kΩ.

Approx. 1 Hz den  
Filtren  
geçirmeye başlar

DC blockmp. lowpass


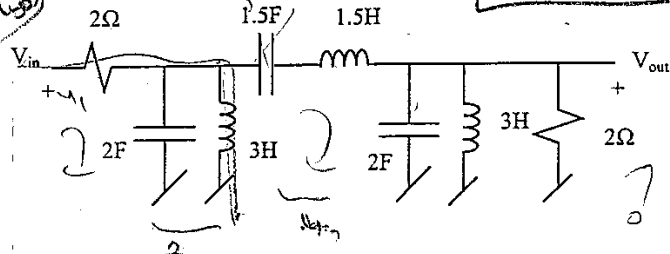
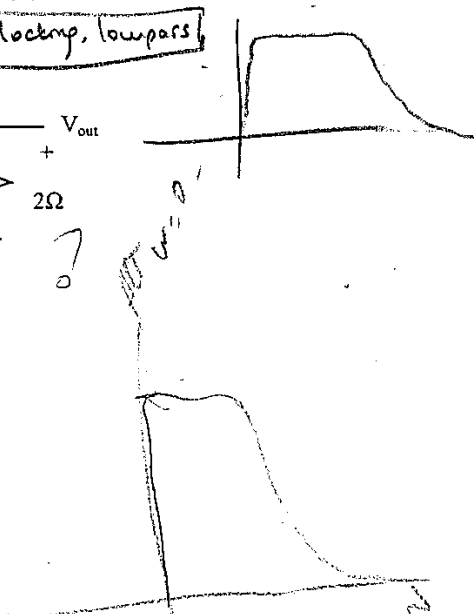


Figure 2

$$q_1, a_0$$


$$2\pi \cdot 10^6$$

$$10^6$$

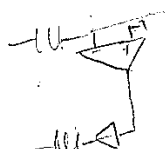


1) a)  $(v_2 - v_1) \cdot \frac{1}{R} = -v_3 sC \Rightarrow \frac{v_3}{(v_1 - v_2)} = \frac{1}{sRC}$

b)

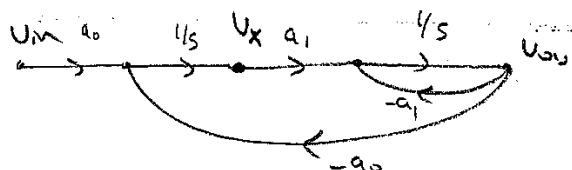

$(v_{in} - v_{out}) \frac{a_0}{s} = v_x \Rightarrow \frac{v_x}{v_{in} - v_{out}} = \frac{a_0}{s} \Rightarrow a_0 = \frac{1}{R_0 C_0}$

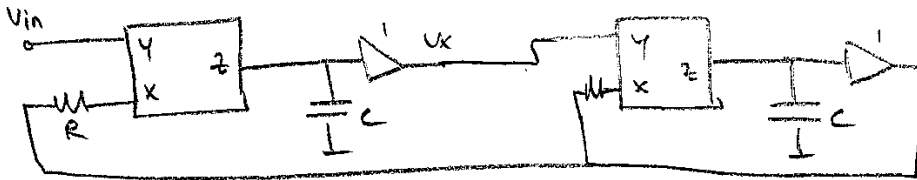$(v_x - v_{out}) \frac{a_1}{s} = v_{out} = \frac{v_{out}}{v_x - v_{out}} = \frac{a_1}{s} \quad a_1 = \frac{1}{R_1 C_1}$



c)  $\frac{v_{out}}{v_{in}} = \frac{a_0 a_1}{s^2 + a_1 s + a_0 a_1}$

$\omega_0 = \sqrt{a_0 a_1} = \sqrt{\frac{1}{R_0 R_1 C_0 C_1}} \Rightarrow \frac{1}{\sqrt{R_0 R_1 C_0 C_1}} = 2\pi \cdot 10^5$

$\frac{\omega_0}{Q} = a_1 \Rightarrow Q = \frac{a_0}{a_1} = \sqrt{\frac{R_1 C_1}{R_0 C_0}} = \sqrt{2} \Rightarrow R_1 = R_0 \Rightarrow \frac{C_1}{C_0} = 2 \quad C_1 = 2C_0$

$R_0 C_0 = \frac{1}{2\pi \cdot 10^5}$

$R_0 = 10k \quad C_0 = 0.113 \cdot 10^{-9} = 113 pF$

exakte  $H_{LP} = \frac{K \omega_0^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$




**İTÜ**  
**ELEKTRİK - ELEKTRONİK FAKÜLTESİ**





Soru	1	2	3	4	5	6	7	8	Toplam
Not									

Tarih :      /      /  
Bölüm :  
Ders :  
No :  
Adı Soyadı :  
İmzası :

Dec 17, 2005

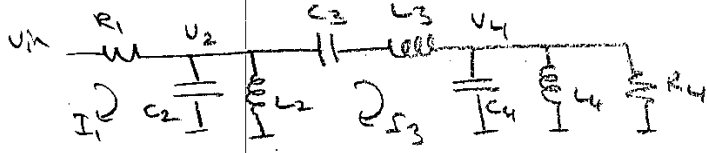

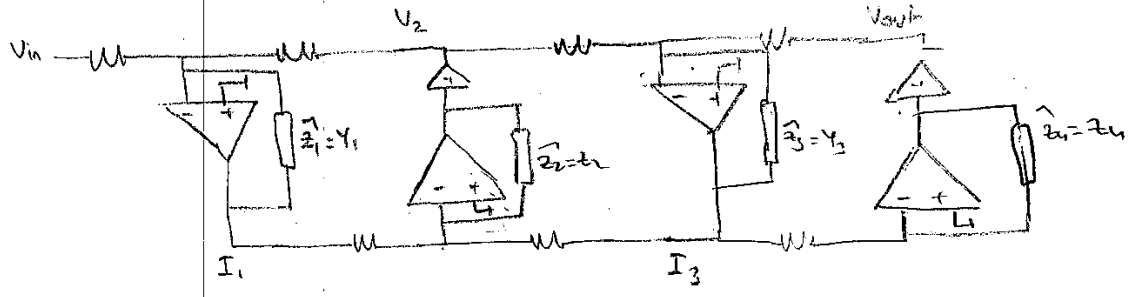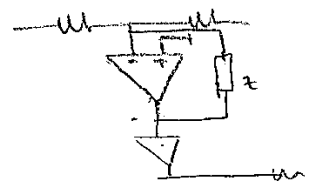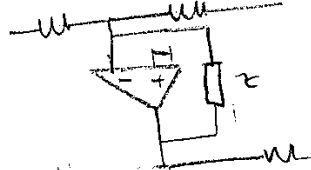
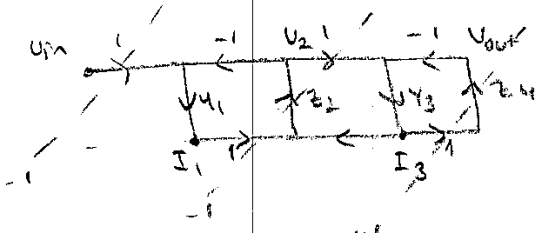
← Not: Burada 1 olmalı -1 ile çarpıyoruz.




$$\hat{z}_1 = Y_1 = 1/R_1 \Rightarrow \frac{1}{sL_1} = 9.5 \Omega$$

$$\hat{z}_3 = Y_3 = \frac{1}{sL_3 + \frac{1}{sC_3}}$$
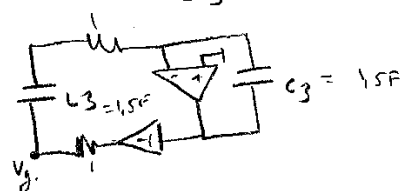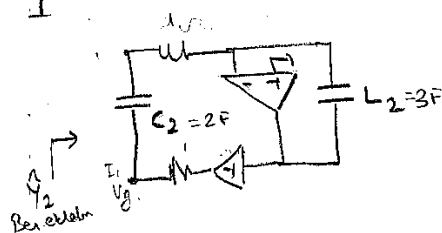
$$\hat{z}_2 = Z_2 = \frac{1}{sC_2 + \frac{1}{sL_2}}$$


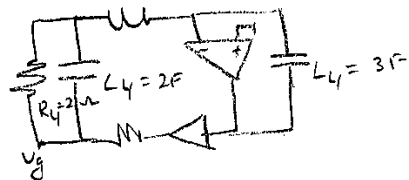
$$\hat{z}_4 = Z_4 = \frac{1}{sC_4 + \frac{1}{sL_4} + \frac{1}{R_4}}$$



b)  $\text{Bütün de\u011ferler} \times \frac{1}{2\pi \cdot 10^6 \cdot 10^3}$

$$L_{\text{emp}} = sL$$

$$C_{\text{emp}} = \frac{1}{s.C}$$

*Bergstrom*

December 26th, 2007

# ACTIVE NETWORK SYNTHESIS

## Midterm Exam

1) The topology in Fig. 1a consists of an (grounded) RC passive network and a current to voltage converter built around two opamps. Using this topology, a second order Butterworth-type highpass filter with a center frequency of 1MHz and Q of  $1/\sqrt{2}$  will be designed.

a) Determine for what type of  $G_{cb} (= I_C / V_{out})$ , the center frequency will be independent of the opamps finite gains. Show that complex-poles can be realised using this filter (Hint: Express the pole-Q of the system in terms of the parameters of RC-network and R).

Assume that, RC-network is chosen as in Fig. 1b.

- ✓ b) Determine component types.
- ✓ b) Determine where to inject the input signal in order to obtain highpass response.
- ✓ c) Show that the filter realizes highpass characteristic.  $\frac{V_{out}}{V_{in}} \propto \omega^2$ .
- d) Find the values of components assuming that all capacitors are 1pF.

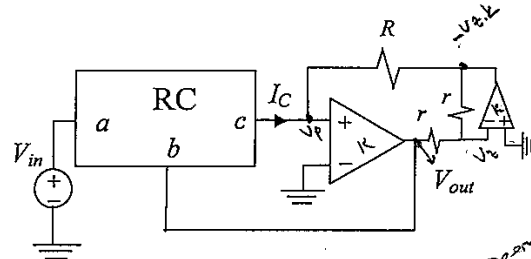


Fig. 1a

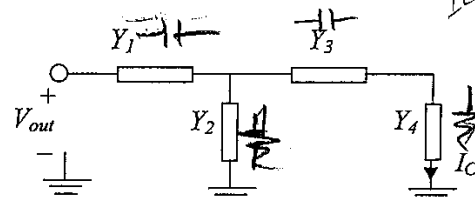


Fig. 1b

2) a) The circuit in Fig. 2 is a second-order lowpass filter with a cut-off frequency of 1 rad/sec. Obtain a fourth-order bandpass filter with a center frequency of 1 rad/sec and  $Q=5$  using lowpass-bandpass transformation. Find an OPAMP-RC circuit realising the bandpass filter.

b) Determine the values of passive components in order to have a cut-off frequency of 10MHz. All R's will be 1kΩ.

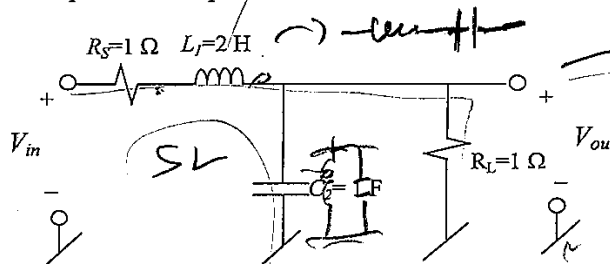


Fig. 2

$$Ks \frac{\omega_p^2}{s^2 + 1} \rightarrow Ks \frac{\omega_p^2}{s^2 + \frac{\omega_p}{Q}s + \omega_p^2}$$

$$s = \frac{\omega}{\omega_p}$$

$$s = \frac{\omega}{\omega_p}$$

$$s = \frac{\omega}{\omega_p}$$


bandpass

December 26, 2007 Midterm  
Socru-1

$G_{cb} = \frac{I_c}{V_{out}}$  common gate adm.  $f_0 = 10^6$   $Q = 1/\sqrt{2}$  highpass filter

Q
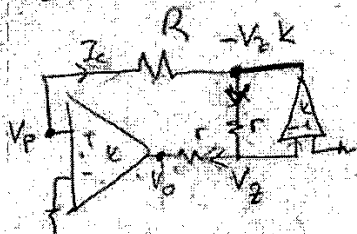
$$I_c = V_{out} G_{cb} + G_{ca} \cdot V_m$$



$$V_p = V_{out}/k$$

$$I_c = \left( \frac{V_{out}}{k} + V_2 k \right) / R$$

$$V_2 - V_o = -V_2 k$$

$$2V_2 + V_2 k = V_o \Rightarrow V_2 (2+k) = V_o$$

$$I_c = \left( \frac{V_{out}}{k} - \frac{V_o k}{2+k} \right) / R$$

$$I_c = V_o \left( \frac{1}{kR} - \frac{k}{(2+k)R} \right)$$

$$I_c = V_o G_{cb} + G_{ca} V_m$$

$$V_o (\alpha - G_{cb}) = G_{ca} V_m$$

$$\frac{V_o}{V_m} = \frac{G_{ca}}{\alpha - G_{cb}} \rightarrow \text{EPF}$$

$$G_{cb} = \frac{n_{cb}}{d(s)} = \frac{\alpha_0 s^2 + a_1 s + a_2}{s^2 + \frac{\omega_1}{q_p} s + \omega_1^2}$$

$$\frac{V_o}{V_m} = \frac{k s^2}{s^2 + \frac{\omega_1}{q_p} s + \omega_1^2}$$

$$F = \frac{G_{ca}}{\alpha - \frac{\alpha_0 s^2 + a_1 s + a_2}{s^2 + \frac{\omega_1}{q_p} s + \omega_1^2}} = \frac{s^2 (\alpha - \alpha_0) + \left( \frac{\omega_1}{q_p} \alpha - a_1 \right) s + (\alpha \omega_1^2 - a_2)}{s^2 + \left( \frac{\omega_1}{q_p} \alpha - a_1 \right) s + (\alpha \omega_1^2 - a_2)}$$


$$\omega_0^2 = \omega_1^2 \text{ ok! } a_0 = a_2 = 0$$

$$\frac{\omega_0}{Q} = \left( \frac{\omega_1}{q_p} \alpha - a_1 \right) / \alpha \Rightarrow$$

$$a_1 = \frac{\omega_0}{q_2} \text{ kugarsok} \Rightarrow Q = \frac{1}{q_p} - \frac{1}{\alpha q_2} \Rightarrow Q = \frac{q_p q_2 \alpha}{\alpha q_2 - q_p}$$

$$G_{cb} = \frac{q_1 s}{s^2 + \frac{\omega_0 s}{q_p} + \omega_0^2}$$

(b)

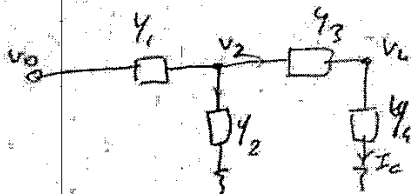

$$(v_0 - v_2)y_1 = I_1$$

$$v_2 \cdot y_2 = I_2$$

$$I_1 = I_2 + I_c$$

$$I_c = I_1 - I_2$$

$$I_c = (v_0 - v_2)y_1 - v_2 y_2$$

$$v_2 \cdot \left( \frac{1}{y_3} + \frac{1}{y_4} \right) = I_c$$

$$I_c = v_0 y_1 - (y_1 + y_2) \frac{(y_3 + y_4)}{y_3 y_4} \cdot I_c$$

$$I_c \cdot \left( \frac{(y_1 + y_2)(y_3 + y_4)}{y_3 y_4} + 1 \right) = v_0 y_1$$

$$\frac{I_c}{v_0} = \frac{y_1 \cdot y_3 y_4}{(y_1 + y_2)(y_3 + y_4) + y_3 y_4}$$

$$= \frac{s^2 C_1 C_4 G_3}{(sC_1 + G_2)(G_3 + sC_4) + sC_4 G_3}$$

$$= \frac{s^2 C_1 C_4 G_3}{s^2 C_1 C_4 + (C_1 G_3 + G_2 C_4 + C_4 G_3)s + G_2 G_3}$$

$$= \frac{s^2 C_1 C_4 G_3}{s^2 C_1 C_4 + (C_1 G_3 + G_2 C_4 + C_4 G_3)s + G_2 G_3}$$

$$= \frac{s^2 G_3}{s^2 + s \left( \frac{C_1 G_3 + G_2 C_4 + C_4 G_3}{C_1 C_4} \right) + \frac{G_2 G_3}{C_1 C_4}}$$

(c)

$$G_{cb} = \frac{s^2 G_3}{s^2 + s \left( \frac{C_1 G_3 + G_2 C_4 + C_4 G_3}{C_1 C_4} \right) + \frac{G_2 G_3}{C_1 C_4}}$$

$$\omega_0 = \sqrt{\frac{G_2 G_3}{C_1 C_4}}$$

$$\frac{\omega_0}{Q_p} = \sqrt{\frac{(C_1 G_3 + G_2 C_4 + C_4 G_3)}{(C_1 C_4)^2}}$$

$$\frac{\omega_0}{Q_p} \cdot G_3 \Rightarrow Q_p = \frac{\omega_0}{G_3} = \sqrt{\frac{G_2 G_3 \cdot \frac{1}{G_3}}{C_1 C_4}} \Rightarrow Q_p = \sqrt{\frac{G_2}{C_1 C_4 G_3}}$$

$$Q_p = \sqrt{\frac{(C_1 C_4)^2 \cdot G_2 G_3}{s^2 C_1 C_4 + (C_1 G_3 + G_2 C_4 + C_4 G_3)s + G_2 G_3}}$$

$$Q = \frac{Q_p Q_2}{Q_p Q_2 - 1} = \frac{1}{\sqrt{2}}$$

$$\omega_0 = 2\pi \cdot 10^6 = \sqrt{\frac{G_2 G_3}{1 \cdot 10^{-24}}} \Rightarrow G_2 G_3 = 4\pi^2 \cdot 10^{-12}$$

$$\frac{1}{R_2} \cdot \frac{1}{R_3} = 4\pi^2 \cdot 10^{-12} \Rightarrow R_2 R_3 = \frac{1}{4\pi^2} \cdot 10^{12} = 0.015 \cdot 10^{12} = 15 \times 10^9$$

(d)



$$C_2 C_3 = 39,47 \times 10^{-12}$$

$$R_2 = R_3 = 1,58 \times 10^5$$

$$q_2 = \sqrt{\frac{C_2}{C_3} \cdot \frac{1}{10^{-24}}}$$

$$q_2 = 10^{12}$$

$$q_p = \sqrt{\frac{C_1 C_4 \cdot C_2 \cdot C_3}{(C_1 C_3 + C_2 C_4 + C_4 C_3)^2}}$$

$$q_p = \frac{2\pi \cdot 10^{-18}}{C_1 C_3 + C_2 C_4 + C_4 C_3} = \frac{2\pi \cdot 10^{-6}}{C_3 + C_2 + C_3} = \frac{2\pi \cdot 10^{-6}}{3 \cdot 2\pi \cdot 10^{-6}}$$

$$Q = \frac{\frac{1}{3} \cdot 10^{12} \cdot \alpha}{\alpha \cdot 10^{12} - \frac{1}{3}} = \frac{1}{\sqrt{2}}$$

$$q_p = \frac{1}{3}$$

$$0,67 \alpha \cdot 10^{12} = 10^{12} - \frac{1}{3}$$

$$\frac{1}{3} = 0,53 \alpha \cdot 10^{12} \Rightarrow 0,62 \times 10^{-12} = \alpha$$

$$\alpha = \left( \frac{1}{k} - \frac{k}{2+k} \right) \frac{1}{\frac{R}{1\Omega}}$$

$$\frac{1}{k} - 1 = \alpha$$




$$\frac{1-k}{k} = \alpha = 10^{-12} \cdot 0,62$$

$$\frac{k}{1-k} = \alpha$$

$$k = \frac{1}{\alpha+1} \Rightarrow k = 1$$


Dec 26th 2007

2.)

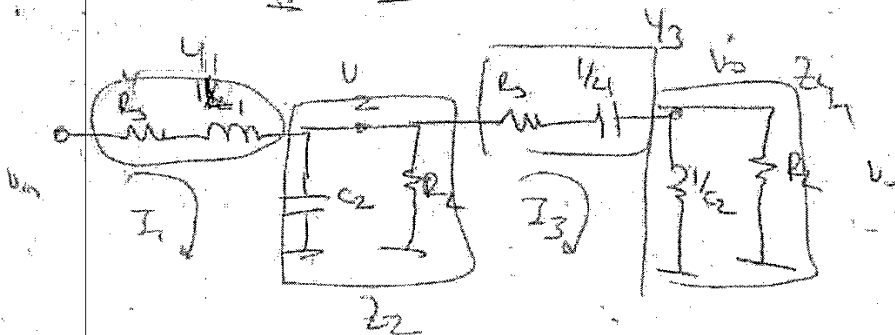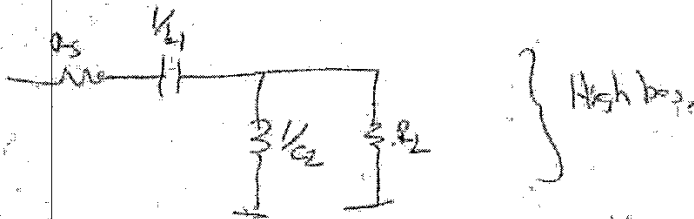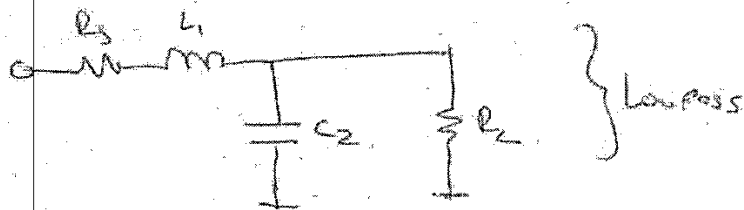


$$I_1 = (V_{in} - V_2) Y_1 \quad V_2 = (I_1 - I_3) Z_2 \quad Y_1 = Y_1 = \frac{1}{R_s + sL_1} \quad Z_2 = Z_2 = \frac{1}{\frac{1}{R_L} + sC_2}$$
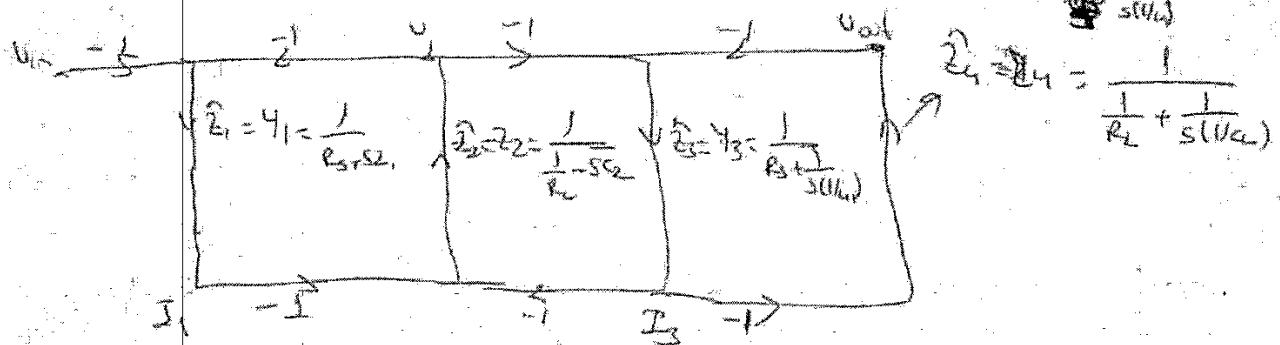
$$I_3 = (V_2 - V_o) Y_3 \quad V_o = I_3 Z_4 \quad Y_3 = Y_3 = \frac{1}{R_s + \frac{1}{s(C_1 + \frac{1}{R_L})}} \quad Z_4 = Z_4 = \frac{1}{\frac{1}{R_L} + \frac{1}{s(C_1 + \frac{1}{R_L})}}$$




$$\hat{Z}_1 = Y_1 = \frac{1}{R_s + sL_1}$$
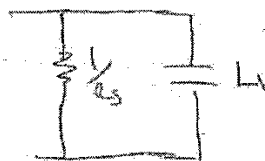
$$\hat{Y}_1 = \frac{1}{Z_1} = R_s + sL_1$$




$$\hat{Z}_2 = Z_2 = \frac{1}{\frac{1}{R_L} + sC_2}$$
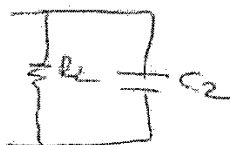
$$\hat{Y}_2 = \frac{1}{Z_2} = \frac{1}{R_L} + sC_2$$



$$\hat{Z}_3 = Y_3 = \frac{1}{R_s + \frac{1}{s(C_1 + \frac{1}{R_L})}}$$

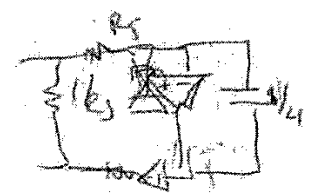
$$\hat{Y}_3 = \frac{1}{Z_3} = R_s + \frac{1}{s(C_1 + \frac{1}{R_L})}$$



$$\hat{Z}_4 = Z_4 = \frac{1}{\frac{1}{R_L} + \frac{1}{s(C_1 + \frac{1}{R_L})}}$$
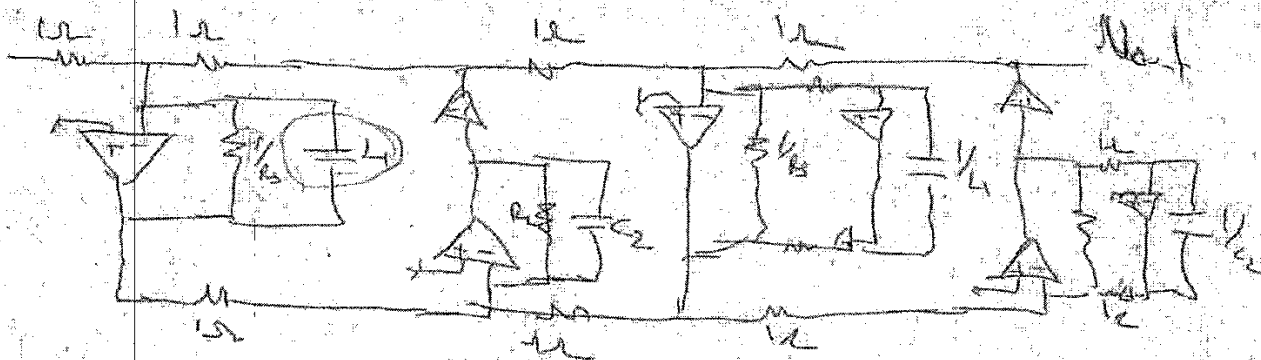
$$\hat{Y}_4 = \frac{1}{Z_4} = \frac{1}{R_L} + \frac{1}{s(C_1 + \frac{1}{R_L})}$$





$$C_n = C_{\text{load}}$$

$$2\pi f_0 = \omega_{\text{load}} / \text{se}$$

$$f_0 = 0,159$$

$$\omega_0 = \frac{10 \cdot 10^6}{0,159} = 62,89 \cdot 10^6$$

$$C = \frac{C_n}{\omega_0 R_0}$$

$$R = \frac{R_n}{R_p}$$

$$R_n = \frac{R}{R_0}$$

$$R = R_n R_0$$

$$R_{1/25} = 1K$$

$$R_2 = 1K$$

$$C_1 = \frac{2}{62,89 \cdot 10^6 \cdot 10^3} = 31,8 \text{ pF}$$

$$C_2 = \frac{1}{62,89 \cdot 10^6 \cdot 10^3} = 15,9 \text{ pF}$$

$$C_{1/21} = \frac{0,5}{\dots} \approx 8 \text{ pF}$$

$$C_{1/22} = \frac{1}{\dots} = 15,9 \text{ pF}$$